

UNIVERSITY OF SWAZILAND
MAIN EXAMINATION, SECOND SEMESTER MAY 2013
FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT OF ELECTRICAL AND ELECTRONIC
ENGINEERING

TITLE OF PAPER: POWER ELECTRONICS
COURSE CODE: EE422

TIME ALLOWED: THREE HOURS

INSTRUCTIONS:

1. There are five questions in this paper. Answer any **FOUR** questions.
Each question carries 25 marks.
2. If you think not enough data has been given in any question you may assume any reasonable values.

**THIS PAPER SHOULD NOT BE OPENED UNTIL PERMISSION
HAS BEEN GIVEN BY THE INVIGILATOR**

THIS PAPER CONTAINS SIX (6) PAGES INCLUDING THIS PAGE

QUESTION ONE (25 marks)

- (a) A switch in a power converter is a BJT having the following parameters.

$$t_{rl} = t_{fl} = 200ns \quad t_{rv} = t_{fv} = 100ns \quad t_{d(on)} = t_{d(off)} = 100ns$$

$$V_{CE(sat)} = 1.5V \quad \theta_{ja} = 1^{\circ} \frac{C}{W} \quad T_{j(max)} = 170^{\circ}C$$

$$T_{amb} = 25^{\circ}C$$

You may assume usual notation.

The load current in the BJT is 30A and the transistor is driven by a square wave signal with 50% duty cycle. The collector voltage is 150V.

- (i) Draw the voltage and current waveforms (linearised) for one switching cycle and mark the relevant parameters.

(5 marks)

- (ii) Find the device power dissipation in terms of frequency.

(8 marks)

- (iii) Determine the maximum switching frequency if the device is operating in free air.

(6 marks)

- (b) The base drive circuit of a BJT consists with a source providing a voltage signal of $-8V$ to $+8V$. This source is connected to the base in series with a 50Ω resistance. Find the turn on delay time.

$$V_{BE} = 0.7V$$


$$C_{BE} = 3nF$$

$$C_{CB} = 1.5nF$$

(6 marks)

QUESTION TWO (25 marks)

Consider the fully controlled bridge rectifier shown in Figure-Q2. The supply voltage $V_s = 220V_{rms}$ at 50Hz, $R = 10\Omega$, $L = 100mH$ and the delay angle $\alpha = 45^\circ$.

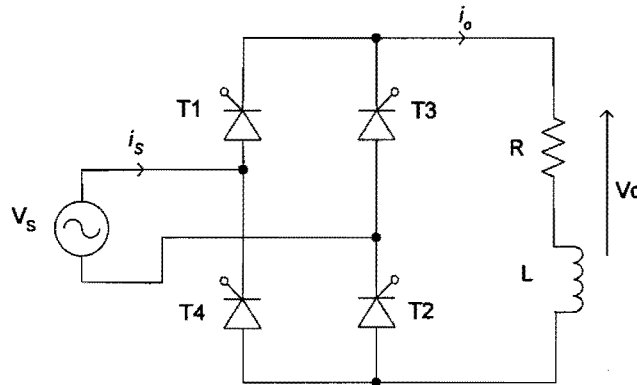**Figure - Q2**

- (a) Show that if the delay angle $\leq \tan^{-1}\left(\frac{\omega L}{R}\right)$, then the current in the load is continuous. (3 marks)
- (b) Verify whether the load current is continuous for the given data. Draw the following waveforms with reference to V_s . (5 marks)
- (i) Load current i_o .
 - (ii) Load voltage v_o .
 - (iii) Currents in the thyristors.
 - (iv) Source current i_s .
- (c) Show that the average load voltage is given by $V_{dc} = \frac{2V_m}{\pi} \cos\alpha$, where α = delay angle and V_m = max. value of V_s . (5 marks)
- (d) Determine the average load voltage and average load current. (2 marks)
- (e) Find the power absorbed by the load and the power factor seen by the source. Consider the effects up to 2nd harmonic. (10 marks)

Note: From the Fourier series expansion,

$$v_o(\omega t) = V_0 + \sum_n V_n \cos(n\omega_0 t + \theta_n); \quad V_n = \sqrt{a_n^2 + b_n^2}$$

$$a_n = \frac{2V_m}{\pi} \left[\frac{\cos(n+1)\alpha}{(n+1)} - \frac{\cos(n-1)\alpha}{(n-1)} \right]$$

$$b_n = \frac{2V_m}{\pi} \left[\frac{\sin(n+1)\alpha}{(n+1)} - \frac{\sin(n-1)\alpha}{(n-1)} \right] \quad n = 2, 4, 6, \dots$$

QUESTION THREE (25 marks)

A three phase uncontrolled half wave rectifier is shown in Figure-Q3. The rectifier is supplied from a $400V_{rms}$, $50Hz$ three phase supply and feeds a resistive load of 5Ω . Assume the phase sequence as a, b, c . Use the sheets provided at the end of the paper for drawing the waveforms.

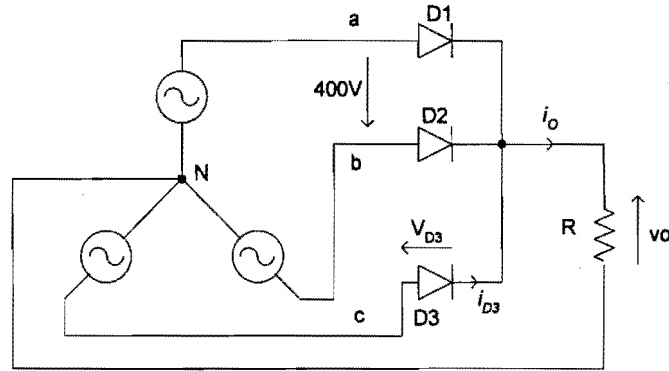


Figure - Q3

- (a) Draw the following waveforms.
- The output voltage v_o and the output current i_o for one input period showing important values. (2 marks)
 - The phase voltage and phase current of phase 'c' for one input period. (4 marks)
 - The diode voltage v_{D3} and the current i_{D3} . (4 marks)
- (b) Determine the following.
- Frequency of the harmonic current having highest amplitude
 - Average dc output voltage and the average dc output current. (5 marks)
- (c) Find the value of inductor which can be used to limit the p-p ripple current to less than 5% of the I_{dc} . State your assumptions. (10 marks)

Note:
$$v_o = V_m \frac{3}{\pi} \sin \frac{\pi}{3} \left(1 - \sum_n^{\infty} \frac{2}{n^2 - 1} \cos \left(\frac{n\pi}{3} \right) \cos n\omega t \right)$$

Where $n = 3, 6, 12, \dots$

QUESTION FOUR (25 marks)

A dc to dc buck converter is shown in Figure-Q4, in which the switching frequency is f and the duty ratio is D .

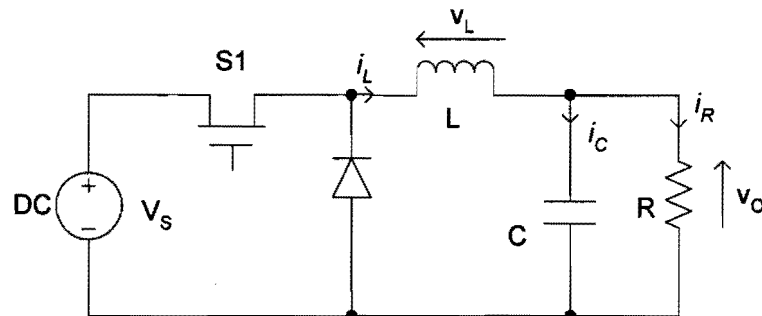
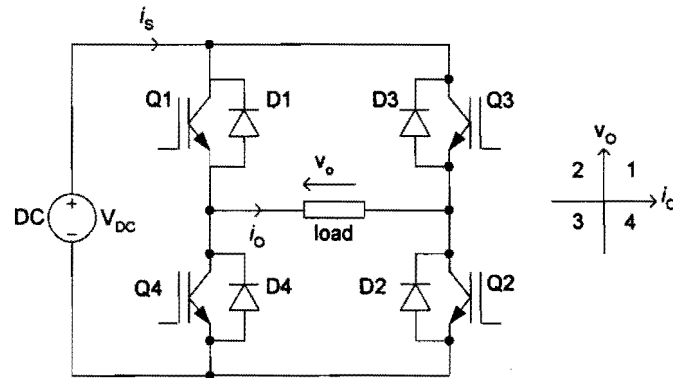


Figure-Q4

- (a) (i) Draw the waveforms of v_L and i_L assuming that the C is large. (2 marks)
- (ii) Show that the peak to peak variation of the inductor current is given by $\frac{V_o(1-D)}{Lf}$ assuming that the V_o is constant. (5 marks)
- (iii) Find an expression for the amplitude of the ripple voltage at the output. (5 marks)
- (iv) Assume the following data for this converter.
 $V_s = 50V$ $D = 0.6$ $L = 450\mu H$ $C = 100\mu F$
 $f = 25KHz$ $R = 25\Omega$
 Calculate the following using the above data.
- The output voltage.
 - Maximum and Minimum inductor currents.
 - The output ripple amplitude.
- (8 marks)
- (b) In a dc to dc boost converter, the supply voltage is 15V. If the load voltage is 24V for a load resistance of 5Ω , find
- the required duty ratio,
 - the average current drawn from the power supply.
- (5 marks)

QUESTION FIVE (25 marks)

The switching arrangement for a full bridge IGBT inverter producing a square wave output voltage is shown in Figure-Q5.

**Figure-Q5**

- (a) Draw the following waveforms assuming that the components are ideal and the load consists of R and L in series. Mark and identify the critical points of the waveforms.
- Load voltage v_o .
 - Load current i_o .
 - Current through Q_1/D_1 and Q_2/D_2 .
 - Current through Q_3/D_3 and Q_4/D_4 .
 - Current through the supply, i_s .
- (10 marks)
- (b) On a drawing of a complete output voltage cycle and with the corresponding output current, mark the devices which are ON in each sub-interval of the cycle specifying the relevant quadrant of operation.
- (5 marks)
- (c) Assume that the switching frequency of this inverter is 50Hz , $V_{DC} = 200\text{V}$, $R = 20\Omega$, and $L = 40\text{mH}$. The load current for the period $0 < t < \frac{T}{2}$ where T is the cycle time, is given by
- $$i_o(t) = \frac{V_{DC}}{R} + \left(I_{min} - \frac{V_{DC}}{R} \right) e^{-\frac{t}{\tau}} ; \quad \tau = \frac{L}{R}.$$
- Determine the answers to the following.
- Maximum and minimum load current values.
 - Power absorbed by the load.
 - Average current in the dc source.


(10 marks)

Name:


Reg. No:

For question three:


Waveform v_O :

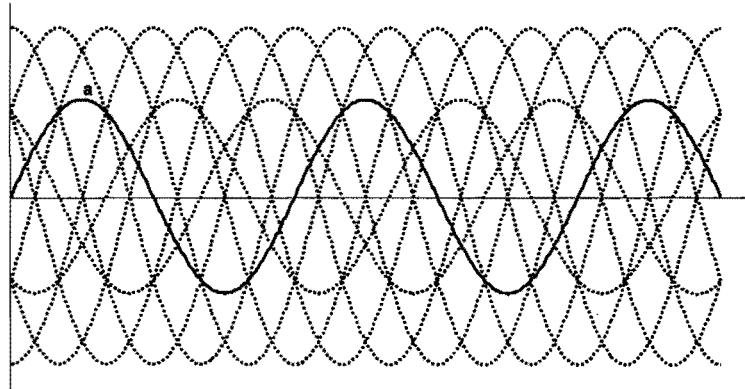

Waveform i_O :

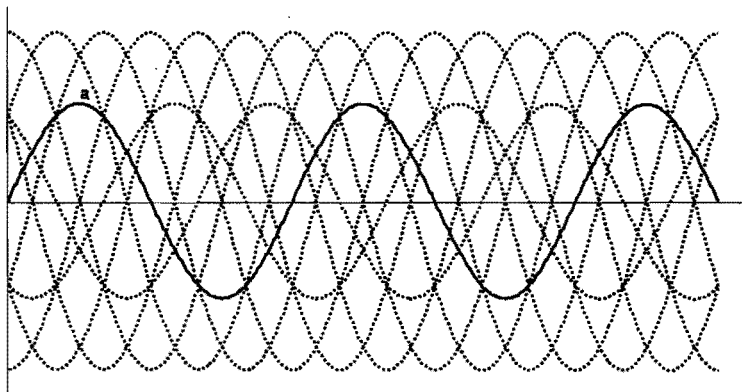

Waveform v_C :

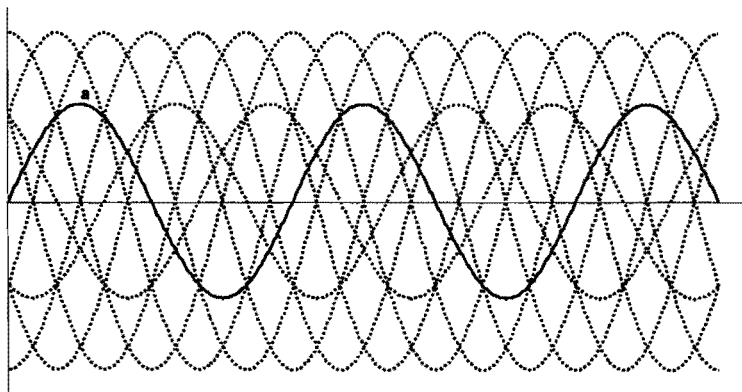


Name:


Reg. No:

For question three:

Waveform i_C :

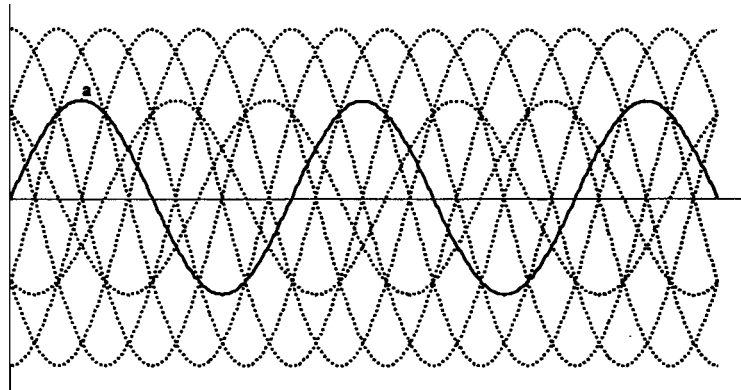

Waveform i_{D3} :

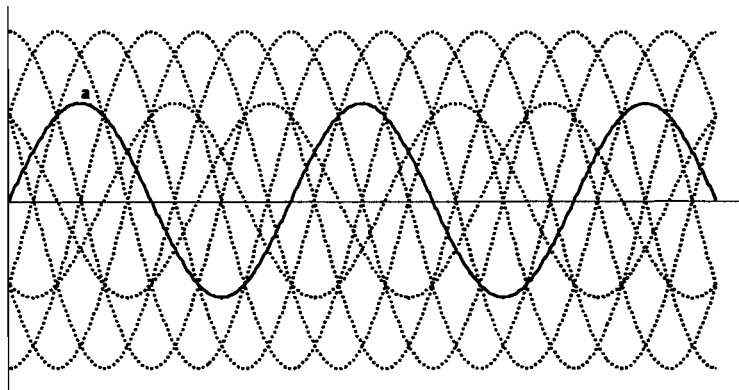

Waveform v_{D3} :

