# University of Swaziland Faculty of Science and Engineering Department of Electrical and Electronic Engineering

### **Main Examination 2014**

Title of Paper:	Analogue Design I
Course Number:	EE321
Time Allowed:	3 hrs

#### **Instructions:**

1

- 1. Answer all four (4) questions.
- 2. Each question carries 25 marks.
- 3. Where appropriate,  $V_{BE} = V_D = 0.7V$ ,  $V_T = 25mV$ .
- 4. E12 range: 1.0, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2

This paper should not be opened until permission has been given by the invigilator.

This paper contains nine (7) pages including this page.

- a) A particular BJT operating at  $I_c = 2mA$  has  $C_{\mu} = 1pF$ ,  $C_{\pi} = 10pF$  and  $\beta = 150$ . Calculate:
  - i)  $f_T$  [5]
  - ii)  $f_{\beta}$  [2]
- b) Using an ideal op-amp, design the inverting low-pass amplifier circuit shown in Fig. 1(a) having a pole frequency of 3kHz.
  [7]



Fig. 1(a)

c) What is the main feature of the differential amplifier?

[1]

d) Consider the common base amplifier shown in Fig. 1(b) with  $R_L = 10k\Omega$ ,

 $R_{C} = 10k\Omega$ ,  $V_{CC} = 10V$  and  $R_{sig} = 100\Omega$ . Note  $I = I_{E}$ .

- i) To what value must I be set in order that the input resistance is  $100\Omega$ ? [5]
- ii) What is the resulting gain from the source to the load? Assume  $\alpha = 1$ ? [5]



iii) In the circuit shown in Fig. 2(a),  $v_{sig}$  is a small sine wave signal with zero average. The transistor  $\beta$  is 100. Note: Do not make any assumptions in this question.



Fig. 2(a)

- i) Find the value of  $R_E$  to establish a dc emitter current,  $I_E$  of about 0.5mA. [5]
- ii) Find  $R_c$  to establish a dc collector voltage,  $V_c$  of about 5V. [3]
- iii) For  $R_L = 10k\Omega$  and the transistor  $r_o = 200k\Omega$ , draw the small signal equivalent circuit of the amplifier and determine its overall voltage gain,  $\frac{v_o}{v_{sig}}$ . [10]
- iv) Differentiate between stagger tuning and synchronous tuning, and for each amplifier
  - sketch the corresponding frequency response. [4]
- v) An op-amp has a slew rate of  $10V / \mu s$ , full-power bandwidth,  $\omega_{M} = 2 \times 10^{6} rad / sec$ . What is the rated output voltage,  $v_{omax}$ ? [3]
- 4

a) Using the topology of Fig. 3(a), design an amplifier to operate between a  $10k\Omega$  source and a  $2k\Omega$  load with an overall gain of -8V/V. The power supply available is 9V. Use a dc emitter current,  $I_E$  of 2mA and a current of about one-tenth of that passes through R1 and R2 in the voltage divider that feeds the base, with the dc voltage,  $V_{Th}$  at the base about one-third of the supply. The transistor available has  $\beta = 100$  and  $V_A = 100V$ . Do not make any assumptions. Use standard resistor values. [15]



- b) A parallel circuit has a capacitor of 100 pF in one branch and an inductor of  $100 \mu H$  plus a resistance of  $10\Omega$  in the second branch. The line voltage is 10V. Find the:
  - i) Resonant frequency,  $f_0$ . [3]
  - ii) Circuit impédance at resonance, Z, . [2]
  - iii) Line current at resonance, *I*. [2]
- c) State 3 advantages of Fixed-Biasing or Base Resistor Biasing [3]

6

a) For the amplifier shown in Fig. 4(a), let  $C_{C1} = 1 \mu F$ .



- i) Find the break frequency,  $f_{p1}$  resulting from  $C_{C1}$ .[5]ii) Given that  $f_{C2} = 15.55Hz$  and  $f_{C_E} = 144.95Hz$ . Calculate the overall the 3-dB low<br/>frequency,  $f_L$  of the amplifier.[2]
- b) Find an expression for the voltage gain,  $\frac{v_{out}}{v_{in}}$  of the circuit in Fig. 4(b). Assume the op-amp is ideal. [4]



c) Consider Fig. 4(c), which shows a capacitor between the input and output terminals.





Using Miller's theorem write equations for the input and output capacitances. [4]

d) The input voltages of an op-amp are  $v_2 = 1005 \mu V$  and  $v_1 = 995 \mu V$ . The op-amp parameters are CMRR = 100 dB and  $A_d = 2 \times 10^5$ . Determine the:

i)	Differential voltage, $v_d$ .	[1]
ii)	Common-mode voltage, $v_c$ .	[1]
iii)	Common-mode gain, $A_c$ .	[4]
iv)	Output voltage, $v_o$ .	[4]

7