

**UNIVERSITY OF SWAZILAND  
SUPPLEMENTARY EXAMINATION, JULY 2015**

**FACULTY OF SCIENCE AND ENGINEERING**

**DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING**

<b>TITLE OF PAPER:</b>	<b>INSTRUMENTATION SYSTEMS</b>
<b>COURSE NUMBER:</b>	<b>EE521</b>
<b>TIME ALLOWED:</b>	<b>THREE HOURS</b>

---

**INSTRUCTIONS:**

1. There are five questions in this paper. **Answer any FOUR questions.**
  2. Each question carries 25 marks.
  3. Marks for different sections are shown on the right hand margin.
  4. Show the steps clearly in all your calculations including any assumptions made. This is because marks may be awarded for method and understanding, even in the event of incorrect answers.
  5. A table of standard values of 1% tolerance resistors and a table of common capacitor values are attached at the end of the question paper for your use in designs.
- 

THIS PAPER IS NOT TO BE OPENED UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR

**THIS PAPER HAS SEVEN (7) PAGES INCLUDING THIS PAGE**

**QUESTION 1 (25 marks)**

- (a) Distinguish between the following terms as used in the characterization of instruments and sensors;

- (i) Accuracy and precision (2 marks)
- (ii) Sensitivity and Resolution (2 marks)
- (iii) Span and range (2 marks)
- (iv) Zero drift and sensitivity drift (2 marks)

- (b) A load cell to be used to measure weight in the range 0 to 12 kg was tested and gave the following output voltages:

Weight, kg	0.0	2.0	4.0	6.0	8.0	10.0	12.0
Output, mV	6.24	7.30	8.48	9.72	10.72	12.04	13.30

- (i) Calculate the sensitivity and zero offset of the load cell. A calculator in linear regression mode may be used and units must be stated. (5 marks)
- (ii) The output of this load cell is to be fed into an analogue-to-digital converter (ADC) chip which has an input analogue signal range of 0 V to 5 V. Design a suitable circuit to interface the load cell to the ADC. (12 marks)

**QUESTION 2 (25 marks)**

Consider the three-opamp configuration of an instrumentation amplifier (IA) shown in Fig. Q2. The amplifier is used for amplifying the output of a differential signal fed in at signal inputs  $v_1$  and  $v_2$ . The opamps A1, A2 and A3 may be assumed to be ideal and the CMRR should be maximized so that  $v_o = k(v_2 - v_1) = kv_{id}$ .

- (a) Derive relevant expressions giving the relationship between the output voltage and the differential input voltage. (9 marks)
- (b) Derive the relationship between the resistors so that maximum CMRR is obtained. (7 marks)
- (c) You are required to design the IA with an overall differential gain of 1000. Practical limitations indicate that the values of the resistors used should be 10 k $\Omega$  or larger. Specify the values of all the resistors you would use in this circuit. (7 marks)

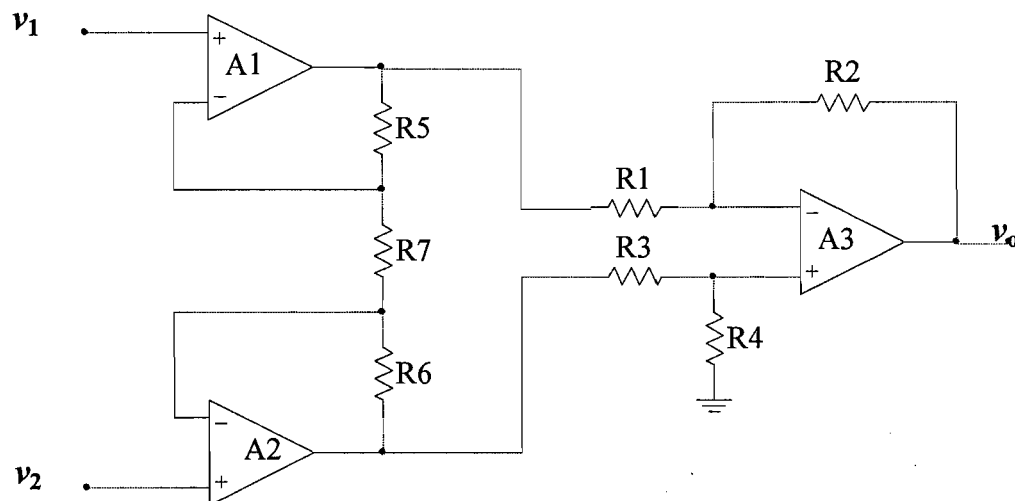




Fig.Q2

- (d) A differential voltage of up to 11 mV peak amplitude is applied at the inputs of the IA. If the amplifiers are capable of producing an output voltage of amplitude to within 1 V of the power supply voltage without saturation, what should be the minimum supply voltage for the amplifiers to operate without clipping the signal. (2 marks)

**QUESTION 3 (25 marks)**

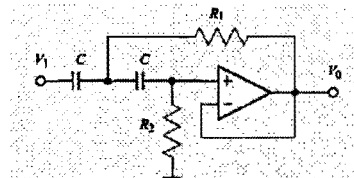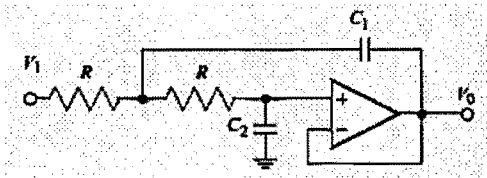- (a) Use the data given below to design a Butterworth **low-pass** four-pole active filter with cut off frequency 15 kHz. (10 marks)

The following data applies to a unity gain Sallen-Key Lowpass and Highpass Configuration active filters. Notice resistors are equal in lowpass and capacitors are equal in Highpass.



Poles	Butterworth		Transitional		Bessel		Chebyshev (0.5 dB)	
	$k_1$	$k_2$	$k_1$	$k_2$	$k_1$	$k_2$	$k_1$	$k_2$
2	1.414	0.707	1.287	0.777	0.907	0.680	1.949	0.653
4	1.082	0.924	1.090	0.960	0.735	0.675	2.582	1.298
	2.613	0.383	2.206	0.472	1.012	0.390	6.233	0.180
6	1.035	0.966	1.060	1.001	0.635	0.610	3.592	1.921
	1.414	0.707	1.338	0.761	0.723	0.484	4.907	0.374
	3.863	0.259	2.721	0.340	1.073	0.256	13.40	0.079
8	1.019	0.981	1.051	1.017	0.567	0.554	4.665	2.547
	1.202	0.832	1.191	0.876	0.609	0.486	5.502	0.530
	1.800	0.556	1.613	0.615	0.726	0.359	8.237	0.171
	5.125	0.195	3.373	0.268	1.116	0.186	23.45	0.044

Source: Brian K. Jones, *Electronics for Experimentation and Research*, Prentice Hall, Englewood Cliffs, NJ, 1986. By permission of Prentice-Hall International (UK) Ltd, London.

Where for **Lowpass**:  $RC_1\omega_c = k_1$  and  $RC_2\omega_c = k_2$ . Higher-order filters use cascaded stages.

For **Highpass**:  $R_1C\omega_c = 1/k_1$  and  $R_2C\omega_c = 1/k_2$ . Higher-order filters use cascaded stages.

- (b) A measurement signal, with frequency 10 Hz, is accompanied by an interference signal with the same amplitude but of frequency 100 Hz. Both signals are passed through a Butterworth filter. It is required that the measured signal emerges with 0.9 of its original amplitude while interference signal emerges with  $1/200^{\text{th}}$  of its original amplitude. Find the minimum order and cut off frequency of the Butterworth filter.

Response of  $n^{\text{th}}$  order Butterworth lowpass filter is given by  $\left| \frac{v_o}{v_{in}} \right| = \frac{1}{\sqrt{1 + \left( \frac{f}{f_c} \right)^{2n}}}$ .

(15 marks)

**QUESTION 4 (25 marks)**

- (a) Consider the half bridge circuit shown in Fig. Q2a

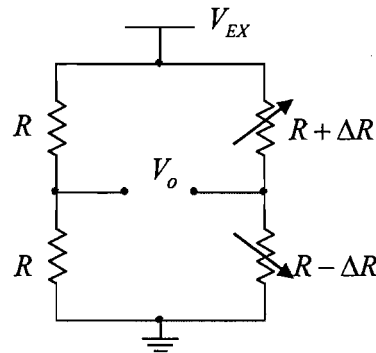


Fig. Q2a

- (i) Derive an expression for the output voltage  $V_o$  of the circuit. (6 marks)
- (ii) Describe using an appropriate sketch how this circuit may be used to remove the temperature error in load measurements based on bending of beams. (5 marks)
- (b) The Steinhart- Hart equation for a thermistor is given by:
- $$\frac{1}{T} = A + B \ln R + C(\ln R)^3, \text{ where } T = \text{Absolute temperature (K)},$$
- $R$  = resistance of the thermistor and  $A$ ,  $B$  and  $C$  are constants
- A typical thermistor has the following coefficients for the Steinhart- Hart equation:  
 $A = 1.1252 \times 10^{-3}/\text{K}$ ,  $B = 2.3478 \times 10^{-4}/\text{K}$ ,  $C = 8.5262 \times 10^{-8}/\text{K}$
- Calculate the temperature in  $^{\circ}\text{C}$  when the resistance of the thermistor is  $3000 \Omega$ .  
 Note that  $0 \text{ K} = -273.15 \text{ }^{\circ}\text{C}$ . (6 marks)
- (c) A CdS cell (LDR) has a dark resistance of  $120 \text{ k}\Omega$  and its resistance in a light beam of  $18 \text{ mW/cm}^2$  is  $30 \text{ k}\Omega$ . The cell has a first-order response time constant of  $60 \text{ ms}$ . We want to trigger a comparator with a threshold voltage of  $1.5 \text{ V}$  within  $30 \text{ ms}$  of the interruption of a  $18 \text{ mW/cm}^2$  beam shone on the cell. Design a circuit to trigger the comparator. (8 marks)

**QUESTION 5 (25 marks)**

- (a) A signal conditioning circuit with four opamps is shown in Fig.Q5a. The nodes 0 are at zero ground potential.

Calculate the voltages expected at all the nodes which have been marked 1 to 10.

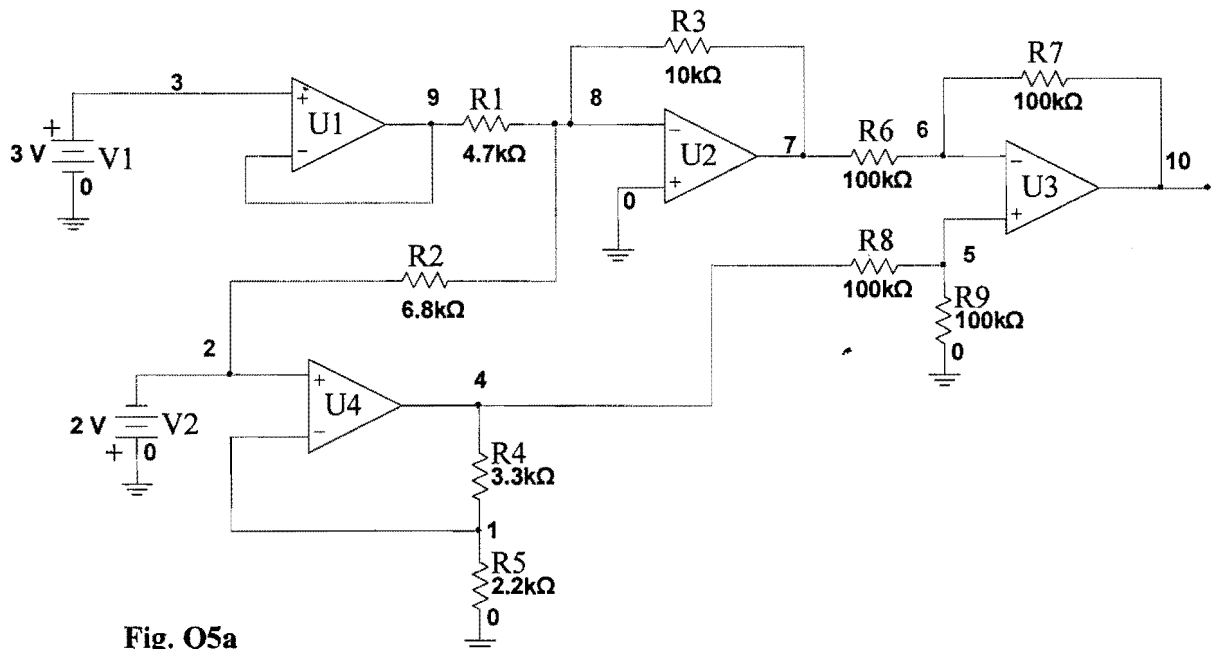


Fig. Q5a

(10 marks)

- (b) A loop current transmitter is based on the circuit in Fig. Q5b. The circuit is required to give an output current  $I_o$  of 2 mA with input voltage  $v_{in}$  of 0 V, and 20 mA with an input voltage of 2 V. The opamp used needs power supplies of  $\pm 15$  V and its saturation occurs at output voltages of  $\pm 13$  V. Complete the design of the circuit by specifying values of  $V_{ref}$ ,  $R$ ,  $R_S$  and maximum value of load resistance  $R_L$ .

(15 marks)

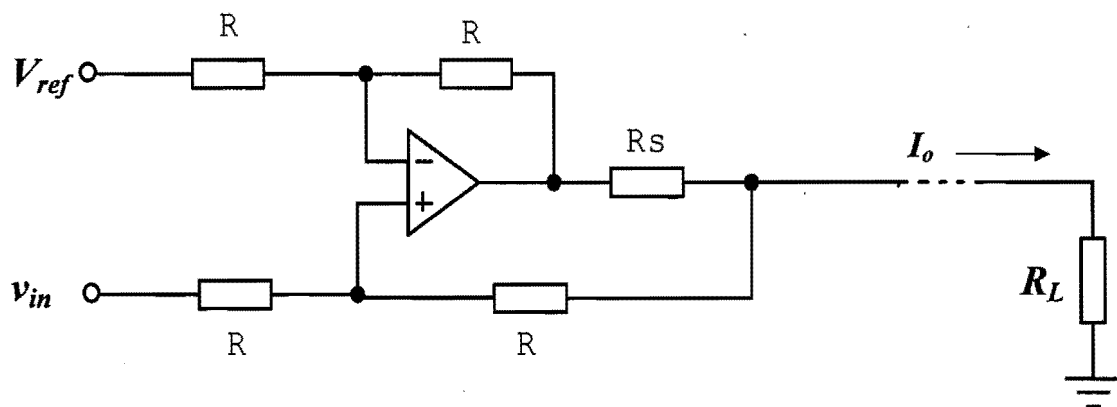


Fig. Q5b

**VALUES OF STANDARD 1% TOLERANCE RESISTORS**

100	140	196	274	383	536	750
102	143	200	280	392	549	768
105	147	205	287	402	562	787
107	150	210	294	412	576	806
110	154	215	301	422	590	825
113	158	221	309	432	604	845
115	162	226	316	442	619	866
118	165	232	324	453	634	887
121	169	237	332	464	649	909
124	174	243	340	475	665	931
127	178	249	348	487	681	953
130	182	255	357	499	698	976
133	187	261	365	511	715	
137	191	267	374	523	732	

d

**COMMON STANDARD VALUES OF CAPACITORS**

10	15	22	33	47	68	pF	Non-polarized
100	150	220	330	470	680	pF	Non-polarized
1	1.5	2.2	3.3	4.7	6.8	nF	Non-polarized
10	15	22	33	47	68	nF	Non-polarized
100	150	220	330	470	680	nF	Non-polarized
1	1.5	2.2	3.3	4.7	6.8	μF	Non polarized /Polarized
10	15	22	33	47	68	μF	(Polarized)
100	150	220	330	470	680	μF	(Polarized)
1000	1500	2200	3300	4700	6800	μF	(Polarized)

$$\text{Butterworth HP filter } \left| \frac{v_o}{v_{in}} \right| = \frac{f/f_c}{\sqrt{1+(f/f_c)^{2n}}}, \quad \text{Butterworth LP filter } \left| \frac{v_o}{v_{in}} \right| = \frac{1}{\sqrt{1+(f/f_c)^{2n}}}$$

$$\text{First order response } a_1 \frac{ds_o}{dt} + a_0 s_o = b_0 s_i \quad \text{or} \quad \tau \frac{ds_o}{dt} + s_o = K s_i \quad \text{and for step response } s_o / s_i = K(1 - e^{-t/\tau})$$