

UNIVERSITY OF SWAZILAND

108

FACULTY OF SCIENCE AND ENGINEERING

DEPARTMENT OF PHYSICS

SUPPLEMENTARY EXAMINATION 2013/2014

TITLE OF PAPER : ELECTRONICS II

COURSE NUMBER : P312

TIME ALLOWED : THREE HOURS

INSTRUCTIONS : ANSWER ANY FOUR OUT OF FIVE QUESTIONS

EACH QUESTION CARRIES 25 MARKS

MARKS FOR DIFFERENT SECTIONS ARE SHOWN IN THE RIGHT-HAND MARGIN.

THIS PAPER HAS 6 PAGES, INCLUDING THIS PAGE.

DO NOT OPEN THE PAPER UNTIL PERMISSION HAS BEEN GIVEN BY THE INVIGILATOR.

QUESTION 1

109

- (a) (i) What is meant by inverse feedback? (3 marks)
- (ii) What is meant by the Barkhausen criterion? (3 marks)
- (b) State the distinct advantages of inverse feedback to an amplifier. (3 marks)
- (c) An amplifier has an open-loop gain of magnitude A. A fraction B of its output signal voltage is fed back to the input so as to subtract from the signal at the input.
- Derive an expression for the overall voltage gain with feedback. (5 marks)
- (d) An amplifier has the following properties:
- Open-loop gain = -500
Feedback is applied with a feedback factor of 0.2
- (i) What is the loop gain? (2 marks)
- (ii) Find the voltage gain with feedback. (2 marks)
- (iii) Determine the percentage fall in gain with feedback if the open-loop gain of the amplifier falls by 20 per cent. (7 marks)

QUESTION 2

10

- (a) (i) Draw the circuit diagram of an astable multivibrator. (2 marks)
- (ii) Explain how the astable multivibrator works and assume that when the d.c. power supply is switched on, current rises faster in transistor T_1 in relation to transistor T_2 . The d.c. supply voltage is 9 V. (6 marks)
- (iii) Sketch the waveforms observed at the base and collector of transistor T_1 to show how the voltage varies with time. (6 marks)
- (b) (i) Write an expression for the frequency of oscillation of a phase shift oscillator that is designed of a BJT amplifier and a phase-shift ladder network. The ladder network is made up of equal resistors and equal capacitors. (2 marks)
- (ii) Consider each of the capacitors to have a fixed capacitance $C = 0.01 \mu\text{F}$ whilst each of the resistances can be varied from $2 \text{ k}\Omega$ to $200 \text{ k}\Omega$.
Calculate the minimum and maximum frequencies which can be generated by the oscillator. (6 marks)
- (iii) Explain why the open-loop gain of the amplifier used in the phase shift oscillator must be of magnitude ≥ 29 . (3 marks)

QUESTION 3

- (a) With the aid of a circuit diagram and appropriate equations, explain how you would measure the input resistance of a device, such as an amplifier. (5 marks)
- (b) Consider an RC low-pass filter with component values $R = 10.61 \text{ k}\Omega$ and $C = 0.015 \text{ }\mu\text{F}$,
- Find the cut-off frequency of the filter, in Hertz. (2 marks)
 - Find the magnitude of v_o when v_i has a frequency 500 Hz, 1 kHz, and 2 kHz. (7 marks)
 - Using the values of v_o calculated in (ii), sketch v_o versus frequency. (3 marks)
- (c) (i) Calculate v_{out} as a function of time for the circuit shown in Fig. 1, given that $v_{in} = A \sin \omega t$, $A = 500 \text{ mV}$ and $\omega = 100 \text{ rad.s}^{-1}$. (4 marks)
- (ii) Sketch graphs of v_{out} and v_{in} against time. (4 marks)

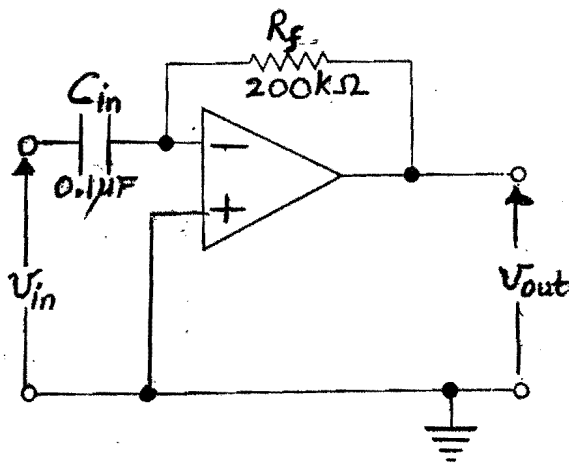


Fig. 1

QUESTION 4

112

- (a) Fig. 2 shows an operational integrator.

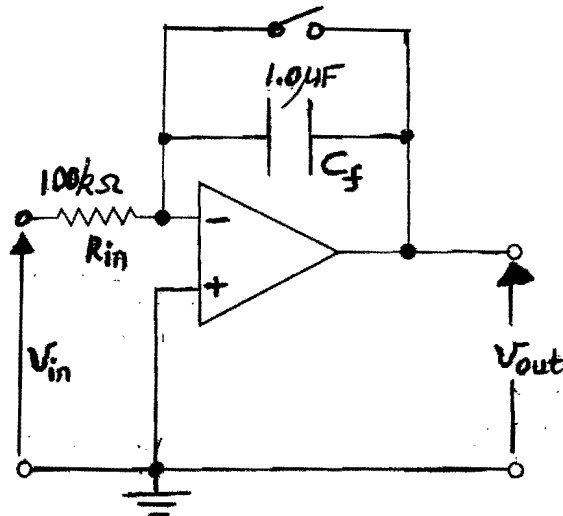


Fig. 2

- (i) What is the relationship between v_{out} and v_{in} for a circuit of this type? (1 mark)
 - (ii) Calculate v_{out} as a function of time if $v_{in} = -10$ mV. Sketch a graph of v_{out} and v_{in} as a function of time. Label the graph. (5 marks)
 - (iv) Calculate v_{out} as a function of time when v_{in} is a sinusoidal waveform with a frequency of 100 Hz and a peak value of 10 V. Sketch v_{out} and v_{in} as a function of time on the same graph. Label the graph. (9 marks)
- (b) Use op-amps to design a circuit which corresponds to the following ideal relationship between the output and input voltages:

$$v_{out} = -(v_{in} - 2 \times 10^{-4} \int v_{in} dt) \quad (10 \text{ marks})$$

QUESTION 5

(13)

(a) Consider the RLC bandpass filter shown in Fig. 3.

- (i) Derive an expression for the magnitude of the transfer function of this filter. (5 marks)
- (ii) Derive the expression for the resonant frequency. (4 marks)
- (iii) Calculate the value of the resonant frequency? (2 marks)
- (iv) What is the Q-factor? (2 marks)
- (v) Find the cut-off frequencies, f_1 and f_2 . (6 marks)
- (vi) Find the bandwidth. (1 mark)

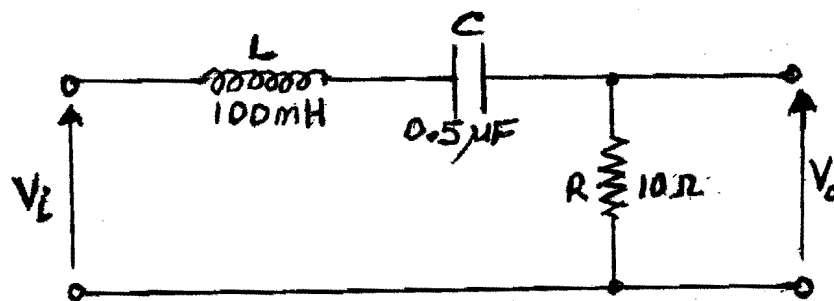


Fig. 3

(b) Calculate the phase difference between v_{out} and v_{in} , for the high-pass filter shown in Fig. 4, given that the frequency of the input voltage is 20 kHz. (5 marks)

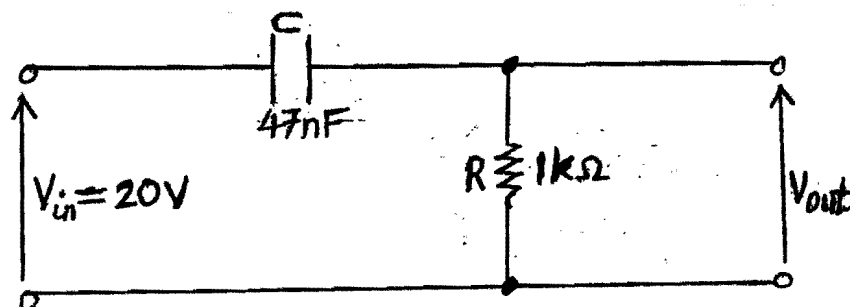


Fig. 4